
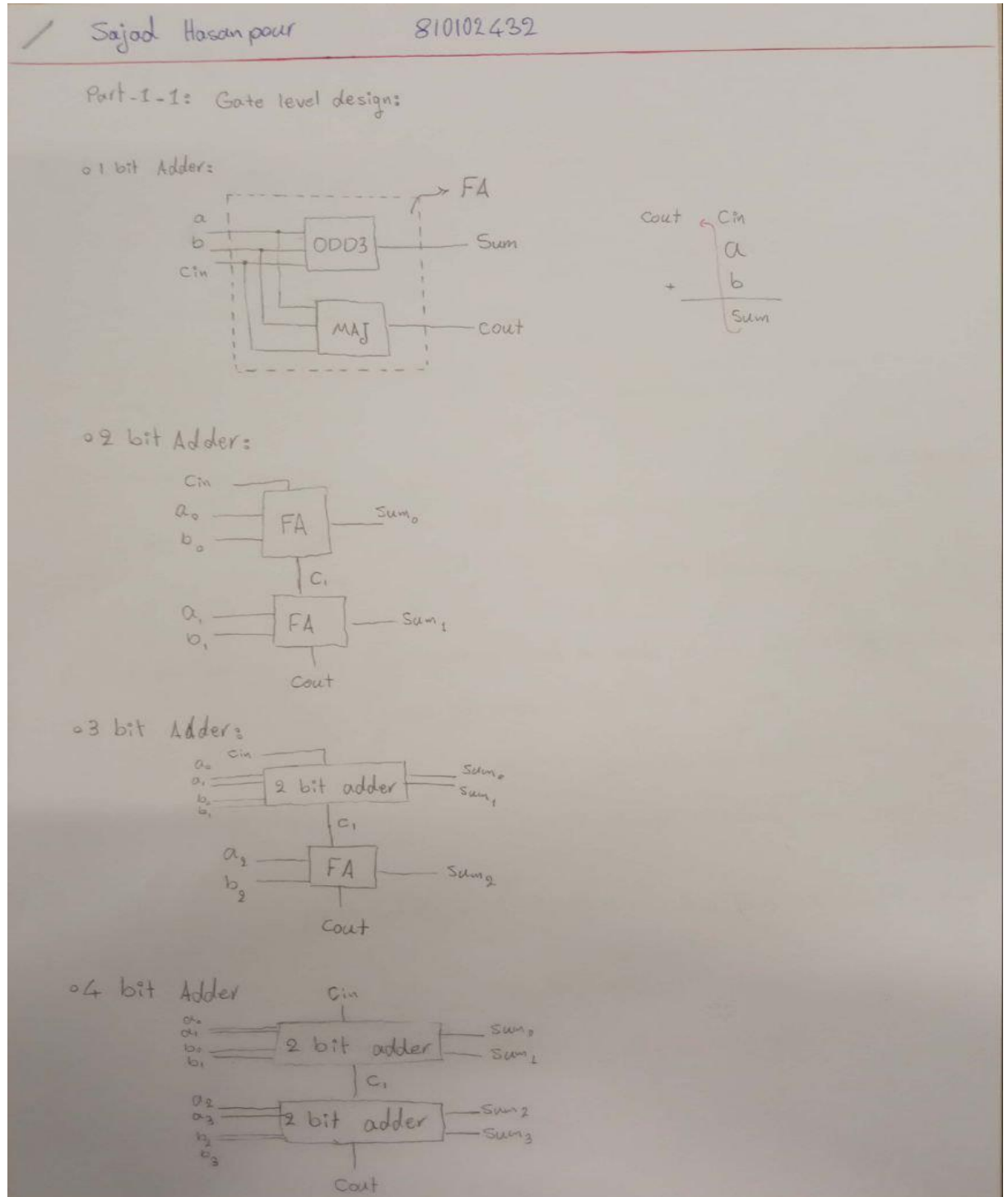


Part1:

1. Gate Level Design:

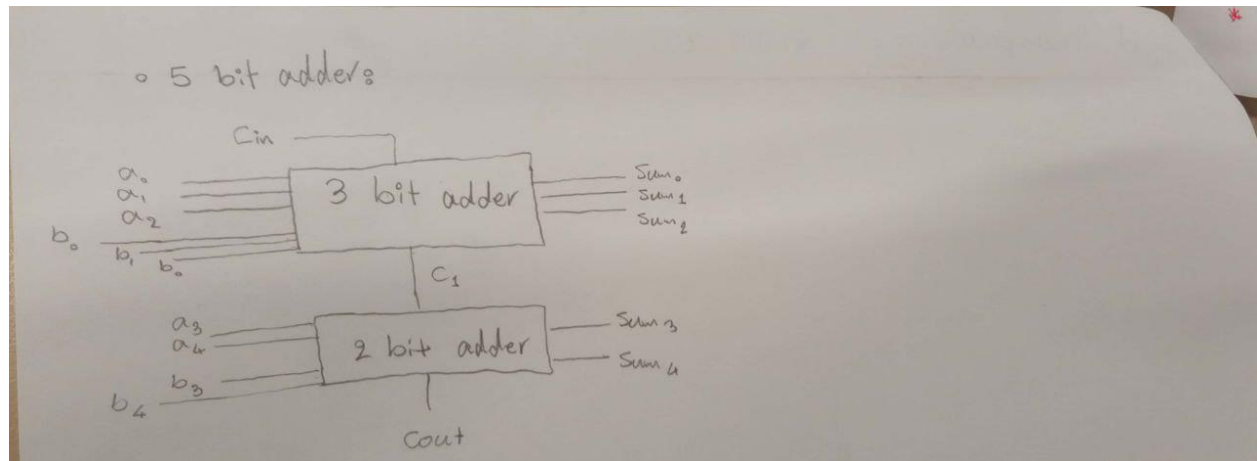

2. System Verilog Modules:

```
module MAJ(input a,b,c,output w);
    assign #(35,36) w=((b&c) | (a&c) | (a&b));
endmodule
```

```
module ODD3(input a,b,c,output w);
    assign #(28,27) w= a^b^c;
endmodule
```

```
module fulladder(input a,b,cin,output sum,cout);
    Odd3 odd(a,b,cin,sum);
    Maj3 maj(a,b,cin,cout);
endmodule
```

```
module two_bit_adder(input [1:0]a,b,input cin,output [1:0]sum,output cout);
    wire c1;
    fulladder F1(a[0],b[0],cin,sum[0],c1);
    fulladder F2(a[1],b[1],c1,sum[1],cout);
endmodule
```

```

module three_bit_adder(input [2:0]a,b,input cin, output [2:0]sum,output cout);
    wire c1;
    two_bit_adder T1(a[1:0],b[1:0],cin,sum[1:0],c1);
    fulladder F1(a[2],b[2],c1,sum[2],cout);
endmodule

```

```

module four_bit_adder(input [3:0]a,b,input cin, output [3:0]sum,output cout);
    wire c1;
    two_bit_adder T1(a[1:0],b[1:0],cin,sum[1:0],c1);
    two_bit_adder T2(a[3:2],b[3:2],c1,sum[3:2],cout);
endmodule

```


```

module five_bit_adder(input [4:0]a,b,input cin, output [4:0]sum,output cout);
    wire c1;
    three_bit_adder T1(a[2:0],b[2:0],cin,sum[2:0],c1);
    two_bit_adder T2(a[4:3],b[4:3],c1,sum[4:3],cout);
endmodule


```

3. Simulation and Waveforms:


1-Full adder:

 


2-Two bit adder:

 




3- Three bit adder:

 


4- Four bit adder:

 




5- Five bit adder:

   

Part2:

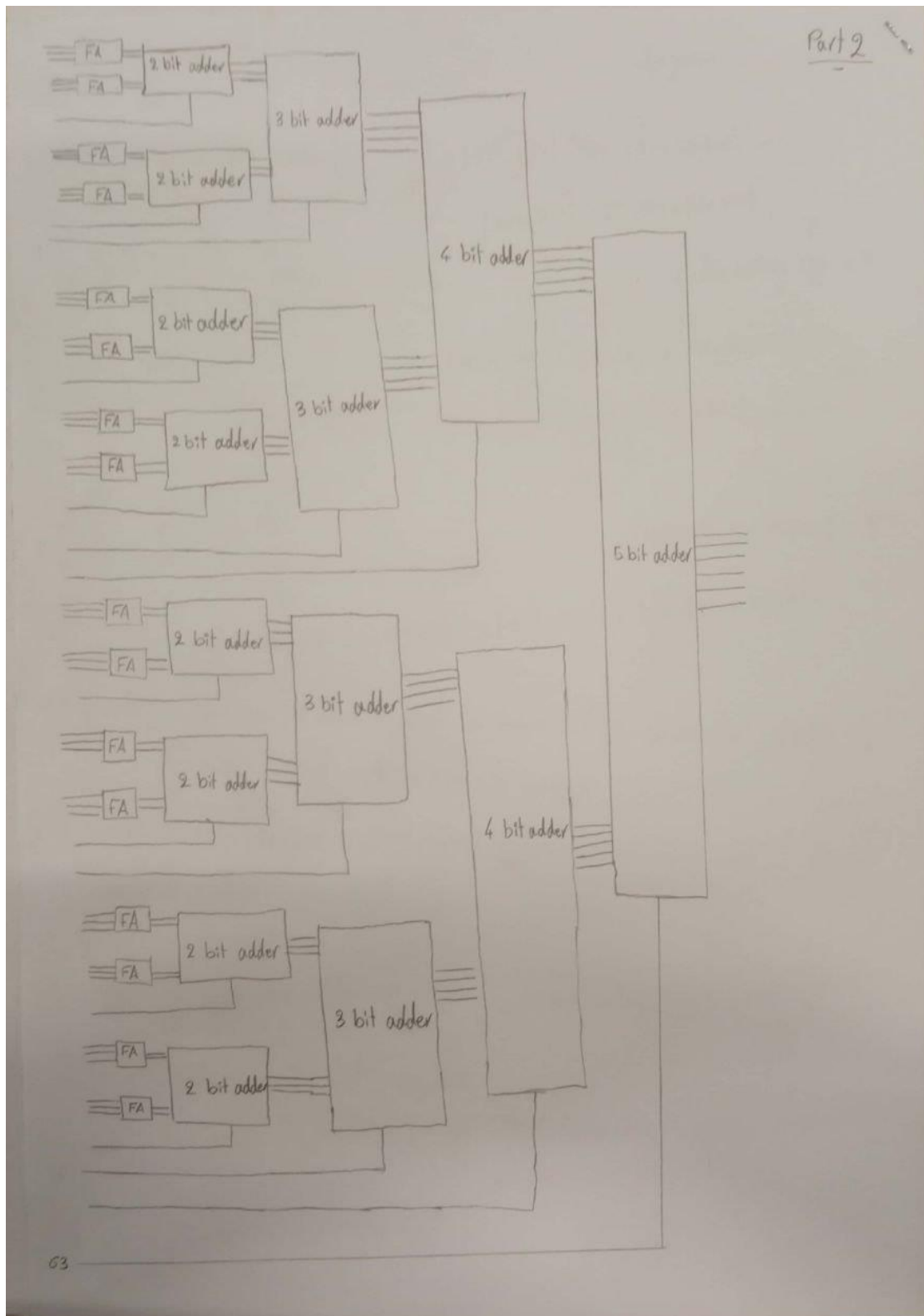

Part2-waveforms:

   



Part3:

* 4 bit adder delay:

$$\text{cout} \Rightarrow (63, 63) + (63, 63) = (126, 126)$$

$$(70, 72) + (70, 72) = (140, 144) \xrightarrow{\text{max}} (140, 144)$$

* 5 bit adder delay:

$$\text{cout} \Rightarrow (98, 99) + (63, 63) = (161, 162)$$

$$\text{sum} \Rightarrow (133, 135) + (70, 72) = (203, 207) \xrightarrow{\text{max}} (364, 369)$$

** 63 input one's Counter:

$$(35, 36) + (70, 72) + (133, 135) + (140, 144) + (364, 369) = \# (742, 756)$$

b_4 b_3 b_2 b_1 b_0
 Cout

Part 3:
 * ODD # (35, 36)
 * MAJ # (28, 27)

* FA delay:
 (worst-case) worst case delay: # (35, 36)

* 2 bit adder: For two bit adder at first we should wait for c answer which is FA
 then we will have another FA delay:

$$\text{Sum1} \rightarrow (35, 36) + (35, 36) = (70, 72)$$

$$\text{Cout} \rightarrow (35, 36) + (28, 27) = (63, 63)$$

$\xrightarrow{\text{max}} 2 \text{ bit delay} = (70, 72)$

* 3 bit adder: one FA and a two bit adder: $C_1 = 2 \text{ bit delay}$

$$\text{Cout} = (63, 63) + (35, 36) = (98, 99)$$

$$(63, 63) + (70, 72) = (133, 135)$$

$\xrightarrow{\text{max}} \# (133, 135)$